
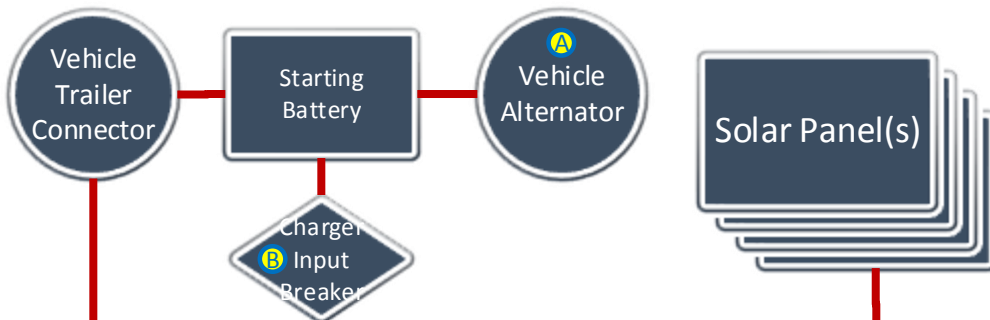


Basic Electrical Diagram for an RV



DC Sources

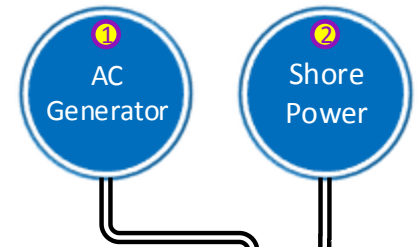





AC Sources




Conversion

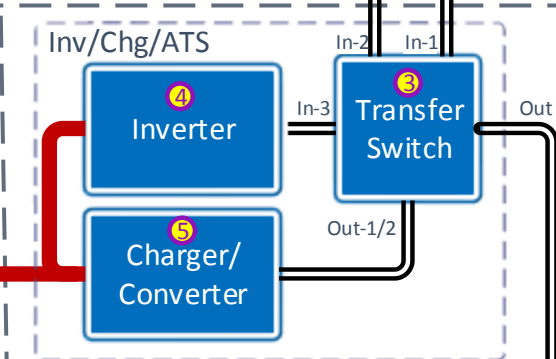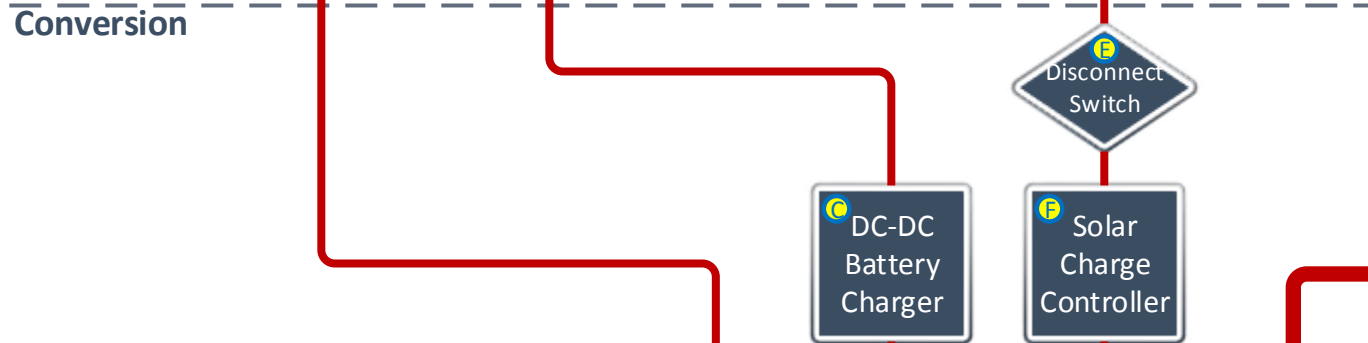

Storage/Distribution/Control

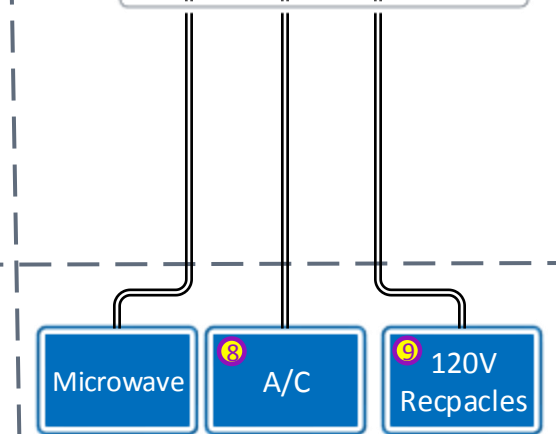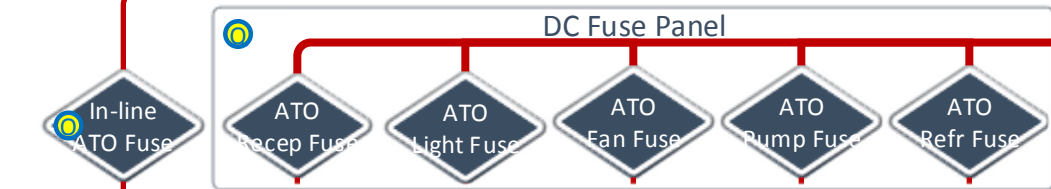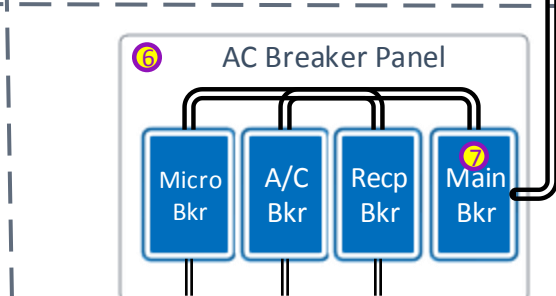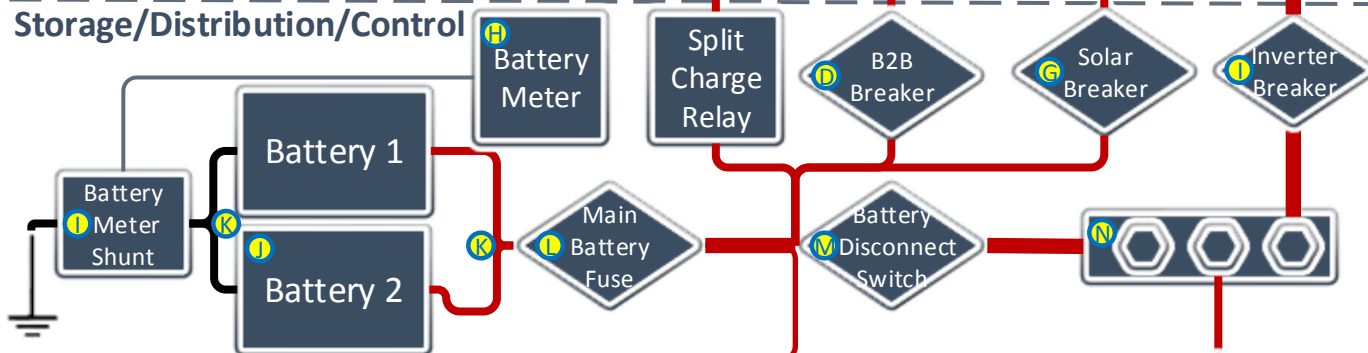

Loads

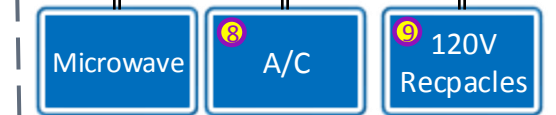

- (A) - Vehicles have either a variable (VVA, 2011 or later) or fixed voltage alternator (FVA). An alternator's 'continuous duty' capacity is about HALF of its 'rated' capacity.
 - (B) – Power cables attached to a battery must have a fuse or breaker near the battery. B2B installation instructions specify the fuse and wire size.
 - (C) – A 'DC-DC charger' (aka 'B2B') is necessary to provide controlled and powerful auxiliary battery charging with a VVA or lithium batteries. Recommend for lead-acid batteries.
 - (D) – If distance is short and cable management good, an Over-Current protective Device (OCPD) here may be omitted but switching may also be desired.
 - (E) – Solar array connection requires switch to remove power for equipment service. A breaker may be used it will have no OCPD function.
 - (F) – The wiring on both sides of the charger may be different. Current is higher on the battery side.
 - (G) – The solar input connection is not cut off by the disconnect switch. To shut off charging (when storing lithium batteries), it is convenient for this to be a breaker not a fuse.
 - (H) – To accurately measure battery state of charge (SOC), a device that uses energy flow rather than just reading battery voltage is necessary.
 - (I) – To measure energy flow in and out of the batteries, measuring both current and voltage (simultaneously) is required. A 'shunt' measures current.
 - (J) – A battery bank can be either lead-acid (LA) or lithium iron phosphate (LFP). There may be multiple batteries in either serial (with 6V 'golf cart' batteries) or parallel connected.
 - (K) – If paralleling multiple LFP batteries, cabling affects equal charging. Use equal length cables on all batteries connecting to a single location.
 - (L) – All battery power flows through single OCPD as close to the battery as possible.
 - (M) – A 'battery disconnect' removes power from all loads except solar and safety sensors. To remove the unswitched loads, turn the breaker off or remove the fuse.
 - (N) – A power distribution block provides a connection point for main load connections. All loads will connect with OCPD as close as possible.
 - (O) – Safety equipment is low power and should never be shut off unless stored. It normally has an in-line fuse somewhere near its connection to battery power.
 - (P) – Detectors may have internal battery back up (usually smoke) and if they are shut down, removing the internal battery is also necessary.
 - (Q) – DC distribution is normally through a panel using ATO/ATC 'automotive' type fuses. Having spare fuses on the capacities used is recommended.
 - (R) – The fuse panel may not be fed by a separate breaker if the connections to the distribution block is close by.
 - (S) – If the refrigerator is an 'absorption' type '2-way' (propane and AC), it still needs DC power to operate controls.
-
- (1) – The AC generator can either be on-board or portable and plugged in to the shore cable.
 - (2) – Shore power can come in as 240V/50A or 120V/30A. Regardless of the input, all of the power is distributed as 120V.
 - (3) – The 'Automatic Transfer Switch' will keep sources separate and route power by priority; 1-Shore, 2-Generator or 3 – Inverter.
 - (4) – The inverter is manually switched on, presumably only when either generator or shore power is not available /desired. Some inverters have integrated charges and ATS.
 - (5) – Charging is a 'smart' function (varies voltage to suit battery charging ~13.5-14.6V) while 'converting' is not (DC power supply @ ~13.8V).
 - (6) - AC power is distributed solely by conventional AC breakers in a rated panel. Even though 240VAC is received on a '50A' connection, it is distributed on 120V lines.
 - (7) – A 'main' breaker protects the source cable from exceeding its capacity.
 - (8) – Branch line breakers supply can supply individual pieces of equipment.
 - (9) - Branch line breakers can supply general purpose receptacle strings strings. GFCI outlets should be used at the beginning of a receptacle string and must in all 'wet' locations